

<b>Semester: September 2020 – January 2021</b>		
<b>Examination: ESE Examination</b>		
<b>Programme code: 01</b> <b>Programme: B.TECH</b>	<b>Class: FY</b>	<b>Semester: I (SVU 2020)</b>
<b>Name of the Constituent College:</b> <b>K. J. Somaiya College of Engineering</b>	<b>Name of the Department</b> <b>COMP/IT</b>	
<b>Course Code: 116U06C107</b>	<b>Name of the Course:</b> Elements of Electrical and Electronics Engineering	
<b>Duration : 1 Hour 45 Minutes</b>	<b>Maximum Marks : 50</b>	
<b>Instructions:</b> <b>1)Draw neat diagrams    2) Assume suitable data if necessary</b>		

Question No.		Max Marks
Q1 (A)	<p>Objective / MCQ type</p> <ol style="list-style-type: none"> <li>✓ 1. Device used to couple input from AC source to rectifier               <ol style="list-style-type: none"> <li>a. Amplifier</li> <li>b. Transformer</li> <li>c. Filter</li> <li>d. Rectifier</li> </ol> </li> <li>✓ 2. The transistor operates in the cut-off region when               <ol style="list-style-type: none"> <li>a. Emitter and collector both junctions forward biased.</li> <li>b. Emitter and collector both junctions reversed biased.</li> <li>c. Emitter junction is forward biased and collector junction is reversed biased.</li> <li>d. Emitter junction is reversed biased and collector junction is forward biased.</li> </ol> </li> <li>✓ 3. Direction of rotation of motor is determined by _____               <ol style="list-style-type: none"> <li>a. Faraday's law</li> <li>b. Lenz's law</li> <li>c. Coulomb's law</li> <li>d. Fleming's left-hand rule</li> </ol> </li> <li>✓ 4. A fan draws 320 mA from a 230V AC supply at 0.75 power factor. Find the active power drawn by the fan?               <ol style="list-style-type: none"> <li>a. 55.2 W</li> <li>b. 55.2 KW</li> <li>c. 73.59W</li> <li>d. 73.59 KW</li> </ol> </li> <li>✓ 5. In pure inductive circuit the current will               <ol style="list-style-type: none"> <li>a. Lag behind the voltage by <math>90^\circ</math></li> <li>b. Leads the voltage by <math>90^\circ</math>.</li> <li>c. Remains in phase with the voltage</li> <li>d. Lag or leads the applied voltage</li> </ol> </li> </ol>	10


	<p>6. ✓ In two wattmeter method, for what value of power factor one wattmeter reads opposite to that of the another</p> <ol style="list-style-type: none"> <li><math>45^0</math></li> <li><math>60^0</math></li> <li><math>90^0</math></li> <li><math>180^0</math></li> </ol> <p>7. ✓ Which part will surely tell that given motor is DC motor and not an AC type?</p> <ol style="list-style-type: none"> <li>Winding</li> <li>Shaft</li> <li>Commutator</li> <li>Stator</li> </ol> <p>8. ✓ Hysteresis loss in transformer is proportional to</p> <ol style="list-style-type: none"> <li><math>f</math></li> <li><math>f^2</math></li> <li><math>f^3</math></li> <li><math>f^{1.5}</math></li> </ol> <p>9. <del>Bandwidth</del> of an ideal operational amplifier is</p> <ol style="list-style-type: none"> <li><del>Low</del></li> <li><del>High</del></li> <li><del>Infinite</del></li> <li><del>Medium</del></li> </ol> <p>10. ✓ Find the Q factor when the voltage across the capacitor is 2000V and the source voltage is 200V.</p> <ol style="list-style-type: none"> <li>10</li> <li>20</li> <li>30</li> <li>40</li> </ol>	
Q1 (B) ✓	<p>Attempt any FIVE questions out of the following (any 5 out of 7)</p> <ol style="list-style-type: none"> <li><del>1. Draw and explain inverting mode of operational amplifier?</del></li> <li>2. Derive the emf equation for single phase transformer.</li> <li>3. An alternating voltage is given by <math>V=141.4 \sin 314t</math>, find frequency, rms value, average value, instantaneous value of voltage at <math>t = 3 \text{ msec}</math>.</li> <li>4. Draw and explain output characteristics of a npn transistor in CE configuration.</li> <li>5. Explain the application of zener diode as a voltage regulator.</li> <li>6. List the advantages of Three Phase AC over single phase AC.</li> <li>7. Draw impedance triangle of a series RLC circuit.</li> </ol>	10

Q2.

a. Find  $I_1$ ,  $I_2$  and  $I_3$  in the given electrical network

---


10

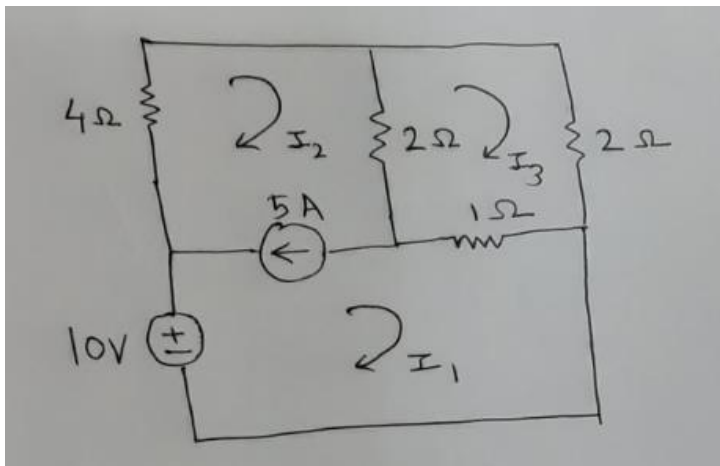

**OR**


a. Calculate power dissipated in  $10\Omega$  using Norton theorem.

05

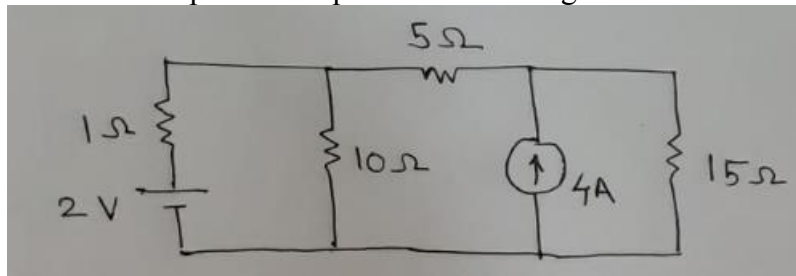

b. Find the Thevenin's equivalent circuit across terminal AB.

05

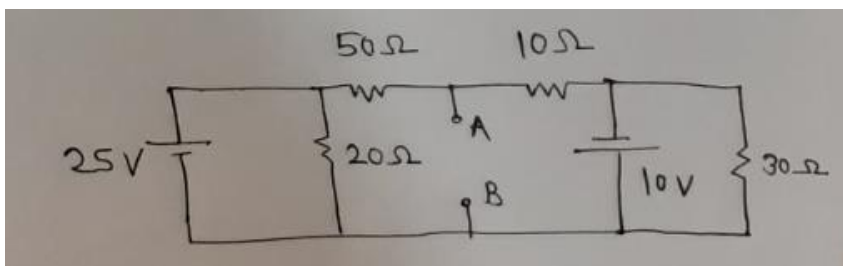

---

Q. 3a

1. A  $100\Omega$  resistor, shunted by a  $0.4\text{H}$  inductor is in series with a capacitor  $C$ . Voltage of  $250\text{V}$ ,  $50\text{Hz}$  is applied to the circuit. Find the value of  $C$  to give unity power factor.

---

05

**OR**

2. A series R-L-C circuit has the following parameter value.  $R=10\Omega$ ,  $L=0.014H$  and  $C=100\mu F$ . Compute the following

- i. Resonant frequency in rad/sec
- ii. Quality factor
- iii. Bandwidth.
- iv. lower and upper frequency points of the bandwidth
- v. maximum values of the voltage appearing across the capacitor, if the voltage  $V(t) = 1 \sin(1000t)$  is applied to the R-L-C circuit.

Q3 b ✓	415 V, 50 Hz, 3 $\Phi$ voltage is applied to three $\Phi$ star connected identical impedances. Each impedance consists of a resistance of $15\Omega$ , capacitance of $177\mu\text{F}$ and inductance of $0.1\text{H}$ in series. Find i. Phase current ii. Line Current iii. Power factor iv. Active Power v. Reactive Power	05
Q4 a. ✓	Draw the phasor diagram considering winding resistance and magnetic leakage when the load is resistive.	05
Q4 b. ✓	Explain full wave bridge rectifier using a capacitor filter.	05