

Supernode Concept

Nodes that are connected to each other by voltage sources but not to the reference node by a path of voltage sources form a super node.

Super node analysis

Ex 1:-

Determine the current in the 5 Ω resistor for the network shown in Fig

Solution Assume that the currents are moving away from the nodes.

Applying KCL at Node 1,

$$10 = \frac{V_1}{3} + \frac{V_1 - V_2}{2}$$

$$\left(\frac{1}{3} + \frac{1}{2}\right)V_1 - \frac{1}{2}V_2 = 10$$

$$0.83 V_1 - 0.5 V_2 = 10 \quad (1)$$

Nodes 2 and 3 will form a supernode.

Writing voltage equation for the supernode,

$$V_2 - V_3 = 20 \quad (2)$$

Applying KCL at the supernode,

$$\frac{V_2 - V_1}{2} + \frac{V_2}{1} + \frac{V_3 - 10}{5} + \frac{V_3}{2} = 0$$

$$-\frac{1}{2}V_1 + \left(\frac{1}{2} + 1\right)V_2 + \left(\frac{1}{5} + \frac{1}{2}\right)V_3 = 2$$

$$-0.5 V_1 + 1.5 V_2 + 0.7 V_3 = 2 \quad (3)$$


Solving Eqs (1), (2) and (3),


$$V_1 = 19.04 \text{ V}$$

$$V_2 = 11.6 \text{ V}$$

$$V_3 = -8.4 \text{ V}$$

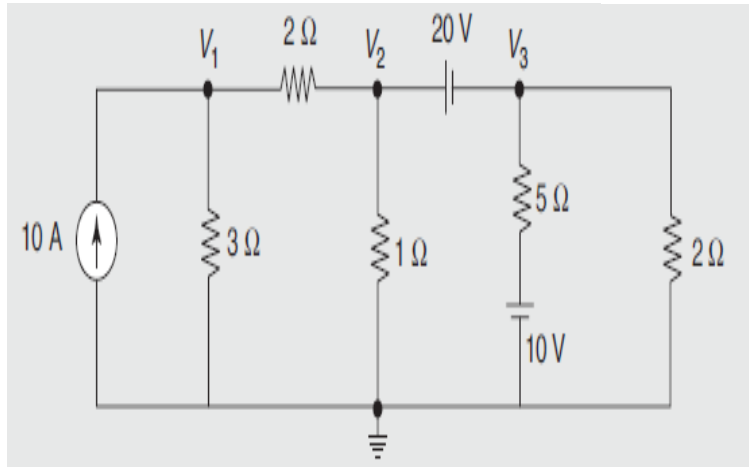
$$I_{5\Omega} = \frac{V_3 - 10}{5} = \frac{-8.4 - 10}{5} = -3.68 \text{ A}$$



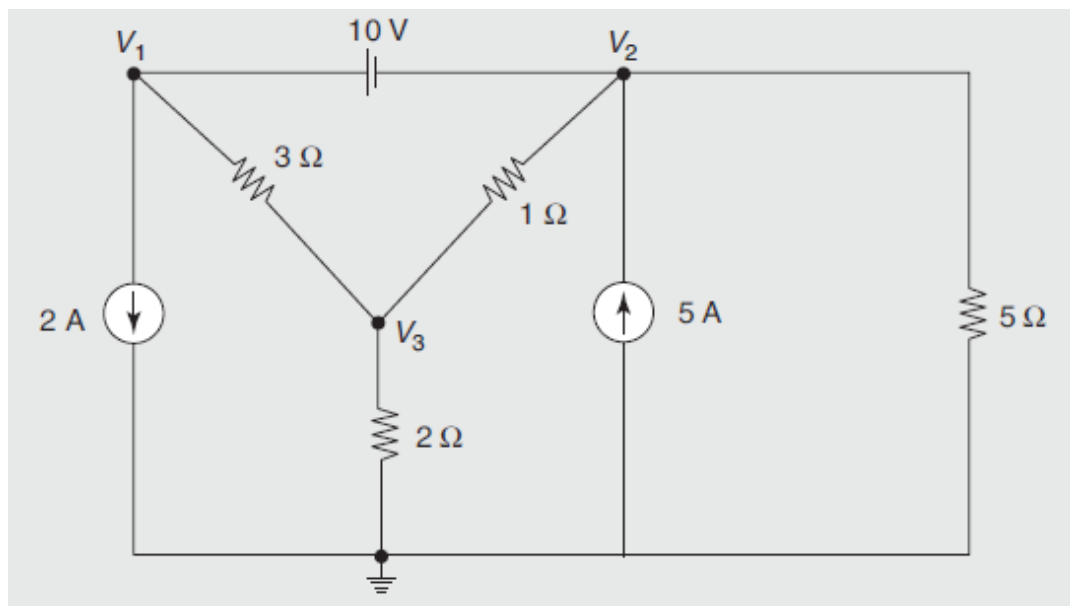

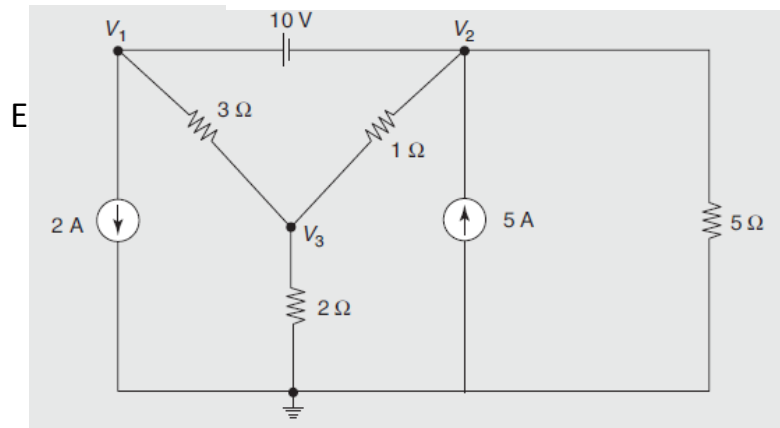Example 2 Find the power delivered by the 5 A current source in the network shown in Fig.

Solution Assume that the currents are moving away from the nodes.



Nodes 1 and 2 will form a supernode.

Writing voltage equation for the supernode,
 $V_1 - V_2 = 10$ (1)

Applying KCL at the supernode,

$$2 + \frac{V_1 - V_3}{3} + \frac{V_2}{5} + \frac{V_2 - V_3}{1} = 5$$

$$\frac{1}{3} V_1 + \left(\frac{1}{5} + 1 \right) V_2 - \left(\frac{1}{3} + 1 \right) V_3 = 3$$

$$0.33 V_1 + 1.2 V_2 - 1.33 V_3 = 3 \quad (2)$$

Applying KCL at Node 3,

$$\frac{V_3 - V_1}{3} + \frac{V_3 - V_2}{1} + \frac{V_3}{2} = 0$$

$$-\frac{1}{3} V_1 - V_2 + \left(\frac{1}{3} + 1 + \frac{1}{2} \right) V_3 = 0$$

$$-0.33 V_1 - V_2 + 1.83 V_3 = 0 \quad (3)$$

Solving Eqs (1), (2) and (3),

$$V_1 = 13.72 \text{ V}$$

$$V_2 = 3.72 \text{ V}$$

$$V_3 = 4.51 \text{ V}$$

$$\text{Power delivered by the 5 A source} = 5 V_2 = 5 \times 3.72 = 18.6 \text{ W}$$

Example 3:-

find the node voltages V_1 , V_2 and V_3 .

Solution Assume that the currents are moving away from the nodes.
Applying KCL at Node 1,

$$4 = \frac{V_1 - V_2}{0.33} + \frac{V_1 - V_3}{0.5}$$

$$\left(\frac{1}{0.33} + \frac{1}{0.5} \right) V_1 - \frac{1}{0.33} V_2 - \frac{1}{0.5} V_3 = 4$$

$$5.03 V_1 - 3.03 V_2 - 2 V_3 = 4$$

(1)

Nodes 2 and 3 will form a supernode.

Writing voltage equation for the supernode,

$$V_3 - V_2 = 5$$

(2)

Applying KCL at the supernode,

$$\frac{V_2 - V_1}{0.33} + \frac{V_2}{0.2} + \frac{V_3}{1} + \frac{V_3 - V_1}{0.5} = 0$$

$$\left(-\frac{1}{0.33} - \frac{1}{0.5} \right) V_1 + \left(\frac{1}{0.33} + \frac{1}{0.2} \right) V_2 + \left(1 + \frac{1}{0.5} \right) V_3 = 0$$

$$-5.03 V_1 + 8.03 V_2 + 3 V_3 = 0$$


(3)

Solving Eqs (1), (2) and (3),

$$V_1 = 2.62 \text{ V}$$

$$V_2 = -0.17 \text{ V}$$

$$V_3 = 4.83 \text{ V}$$

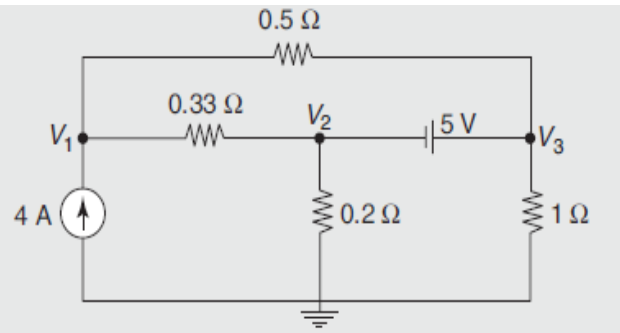

Homework

Find the value of current flowing through the branch ab .

